 



# 1) Implementation of half adder using gate level modeling.

Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Truth table



Schematic

 

Realization

## For Carry

A \ B	0	1
0	0	0
1	0	1

$$\text{Carry} = AB$$

## For Sum

A \ B	0	1
0	0	1
1	1	0

$$\begin{aligned} \text{Sum} &= A\bar{B} + \bar{A}B \\ &= A \oplus B \end{aligned}$$

Fig. 3.12 Maps for half-adder

## DESIGN:

```
module HA(
input a,
input b,
output c_out,
output sum);

xor x1(sum,a,b);
and A1(c_out,a,b);
```

```
endmodule
```

## Testbench:

```
//2Q. gate level implementation of half adder [test bench]
module tb;
```

```
reg in1,in2;
wire sum;
wire carry;
```

```
HA h1 ( .sum(sum), .b(in2),.a(in1),.c_out(carry));
```

```
initial begin
```

```
$monitor (" %b + %b = %b =%d",in1,in2,{carry,sum},{carry,sum});
{in1,in2}=2'b00; #10;
{in1,in2}=2'b01; #10;
{in1,in2}=2'b10; #10;
{in1,in2}=2'b11; #10;
```

```
end
```

```
endmodule
```

## run.do

```
# cd {C:\Users\alisy\Documents\verilog\class1\Q02_half adder}
#environment creation
vlib work
```

```
#compilation
```

```
vlog HA_G.v
```

```
vlog HA_G_tb.v
```

```
#simulation
```

```
vsim work.tb
```

```
run -all
```